

Jaypee Institute of Information Technology, Noida

**T1 Examination, 2022
B.Tech , IV Semester**

Course Title : Digital Systems/ Introduction to Digital Systems Maximum Time : 1 Hr
Course Code : 18B11EC213/15B11EC314 Maximum Marks : 20

- CO 1** Familiarize with the fundamentals of number system, Boolean algebra and Boolean function minimization techniques.
- CO2** Analyze and design combinational circuits using logic gates.
- CO3** Analyze state diagram and design sequential logic circuits using flip flops.
- CO4** Understand the classification of signals & systems and learn basic signal operations and fourier analysis.
- CO5** Understand various steps involved in digitization and transmission of a signal.

- Q1.** Write the BCD code and excess – 3 code of $(987.123)_{10}$. Also write the gray code corresponding to given binary code $(11010001)_2$. [3, CO1]
- Q2.** Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction (a) $X-Y$ and (b) $Y-X$ by using 2's complement method. [2, CO1]
- Q3.** In a new number system A and B are successive digits such that $(AB)_x = 29$ and $(BA)_x = 34$. Find A, B and x. [3, CO1]
- Q4.** Reduce the following expression using K – map and implement the reduced expression using universal NOR gate. [5, CO2]
 $F(A, B, C, D) = \prod M(2, 8, 9, 10, 11, 12, 14)$
- Q5.** Obtain the simplified SOP expression for the function $F(A, B, C) = \sum m(3, 4, 6, 7)$ using Quine Mecluskey method. [4, CO2]
- Q6.** Implement the function $F(A, B, C) = ABC + A'B'C + BC'$ using a single 4×1 Mux. [3, CO2]