

POSSESSION OF MOBILES IN EXAM IS UFM PRACTICE.

Name Vishwakant

Enrollment No. 21108888

Jaypee Institute of Information Technology, Noida
T1 Examination, 2023
B. Tech IV Semester

Course Title: Digital Systems

Course Code: 18B11EC213

Maximum Time: 1 Hr

Maximum Marks: 20

CO1: Familiarize with the fundamentals of number system, Boolean algebra and Boolean function minimization techniques.
CO2: Analyze and design combinational circuits using logic gates.
CO3: Analyze state diagram and design sequential logic circuits using flip flops.
CO4: Understand the classification of signals & systems and learn basic signal operations & Fourier analysis.
CO5: Understand various steps involved in digitization and transmission of a signal.

Note: Attempt all questions. All questions are compulsory.

- Q. 1** (a) Subtract using 10's Complement method: $20 - 100$. [CO1, 1+1+2]
(b) Subtract using 2's Complement method: $(11010)_2 - (1101)_2$.
(c) Simplify the Boolean expression using Boolean laws: $Y = AB + \overline{A}C + A\overline{B}C(AB + C)$
- Q.2.** Find out minimized POS form of the following function: [CO1, 4]
 $F(A, B, C, D) = \sum m(0, 2, 8, 10, 14) + \sum d(5, 15)$ using k-map and also find out EPI's and PI's.
- Q.3.** Implement the function $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$ using 8:1 Mux. [CO2, 4]
- Q. 4** Simplify the function $F(A, B, C) = \sum m(0, 1, 4, 5)$ using QM Techniques [CO1, 4]
- Q.5.** How many decoders are required to construct 6: 64 decoder using 3:8 decoders. Implement the full subtractor using 3: 8 decoders. [CO2, 4]