

# POSSESSION OF MOBILES IN EXAM IS UFM PRACTICE.

Name Vaibhav

Enrollment No. 2110

Jaypee Institute of Information Technology, Noida

T-2 Examination, EVEN 2023  
B. Tech IV Semester

Course Title: Digital Systems  
Course Code: 18B11EC213

Maximum Time: 1 Hr  
Maximum Marks: 20

- CO1: Familiarize with the fundamentals of number system, Boolean algebra and Boolean function minimization techniques.  
CO2: Analyze and design combinational circuit using logic gates.  
CO3: Analyze state diagram and design sequential logic circuits using flip flops.  
CO4: Understand the classification of signals and systems and learn basic signal operations and Fourier analysis.  
CO5: Understand various steps involved in digitization and transmission of signal.

Note: Attempt all questions. All questions are compulsory.

~~Q. 1~~ Convert D flip flop in to JK flip flop.


[CO3, 4]

~~Q. 2~~ Design a 2-bit magnitude comparator using 1-bit magnitude comparator.

[CO2, 4]

~~Q. 3~~ Design the clocked sequential circuit using JK flip flop whose state diagram is shown below:

[CO3, 4]

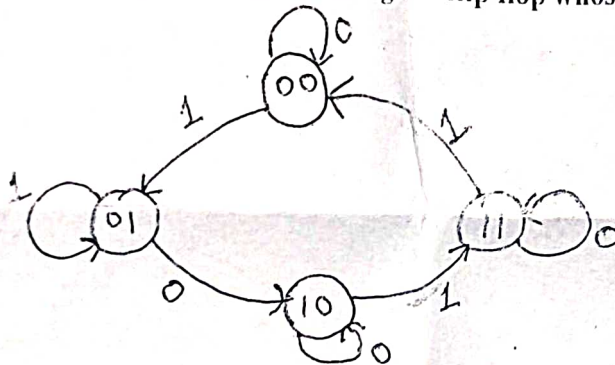

~~Q. 4~~ Design a MOD-5 counter to count the random sequence 0, 1 3, 7, 6. Design should be circulatory to ensure that if we end in any unwanted state, the next clock pulse will reset the counter to zero. Implement the circuit using T-flip flop.

[CO3, 4]

~~Q. 5~~ Design a 4-bit bidirectional shift register with parallel load such that its mode control is as given below. (using 4 x 1 MUX)

[CO3, 4]

| Mode Control |    | Register      |
|--------------|----|---------------|
| S1           | S0 | Operation     |
| 0            | 0  | Parallel load |
| 0            | 1  | No change     |
| 1            | 0  | Shift right   |
| 1            | 1  | Shift left    |